

# 國立彰化師範大學 102 學年度碩士班招生考試試題

系所：工業教育與技術學系

組別：乙組(選考丙)

科目：電路學

☆☆請在答案紙上作答☆☆

共 3 頁，第 1 頁

1. There is no energy stored in the circuit seen in Fig. 1 at the time the two sources are energized. Please find  $v_0$  for  $t > 0$ . (15%)

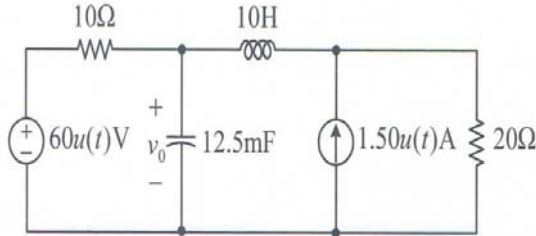


Fig. 1

2. Determine the y-parameters of the two-port circuit shown in Fig. 2. (15%)

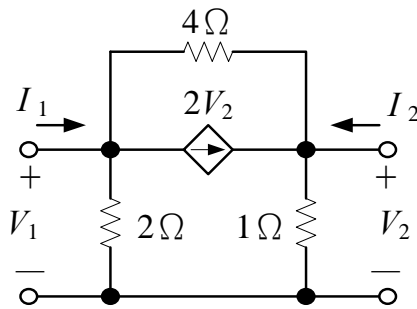


Fig. 2

3. Consider the circuit shown in Fig. 3.

(1) Write the state equation in matrix form 
$$\begin{bmatrix} \frac{d i_L}{dt} \\ \frac{d v_C}{dt} \end{bmatrix} = A \begin{bmatrix} i_L \\ v_C \end{bmatrix} + B v_s. \quad (10\%)$$

- (2) Find the transfer function  $\frac{v_C(s)}{v_s(s)}$ . Let  $v_C(s)$  and  $v_s(s)$  be the Laplace transform of  $v_C$  and  $v_s$ , respectively. (10%)

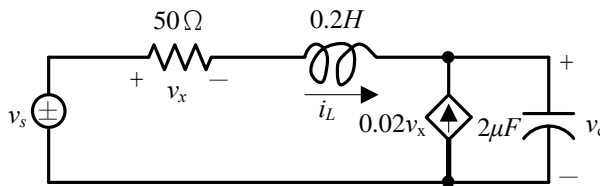


Fig. 3

# 國立彰化師範大學 102 學年度碩士班招生考試試題

系所： 工業教育與技術學系

組別： 乙組(選考丙)

科目： 電路學

☆☆請在答案紙上作答☆☆

共 3 頁，第 2 頁

4. Using mesh analysis,  $L = 2H$ ,  $C = \frac{1}{8}F$ ,  $R = 8\Omega$

- (1) Find the transfer function  $H(s)$ . (5%)
- (2) Find the response  $v(t)$  to  $i_g(t)$  for the circuit. (5%)
- (3) Find the unit impulse response. (5%)
- (4) Find the step response. (5%)

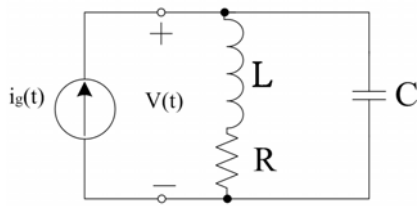


Fig. 4

5. When  $C = 1\mu F$ ,  $R_1 = 1k\Omega$ ,  $R_2 = 1k\Omega$

- (1) Sketch the linearized Bode Gain. (5%)
- (2) Sketch and phase plots. (5%)

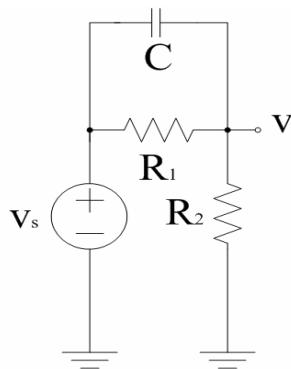


Fig. 5

6. Find  $i(t)$  for  $i_s(t) = 2u(t)$ ,  $C = \frac{1}{12}F$ ,  $L = 2H$ ,  $R_1 = 2k\Omega$ ,  $R_2 = 2k\Omega$ ,  $R_3 = 2k\Omega$ ,  $a = 0.25$ . (10%)

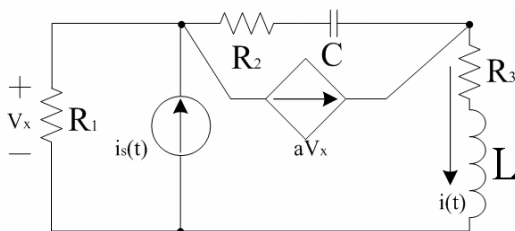


Fig. 6

# 國立彰化師範大學 102 學年度碩士班招生考試試題

系所：工業教育與技術學系

組別：乙組(選考丙)

科目：電路學

☆☆請在答案紙上作答☆☆

共 3 頁，第 3 頁

7. When  $C = \frac{1}{2}F, C = \frac{1}{2}F, L = 1H$ , Investigate the stability of the circuit and sketch the PZD. (10%)

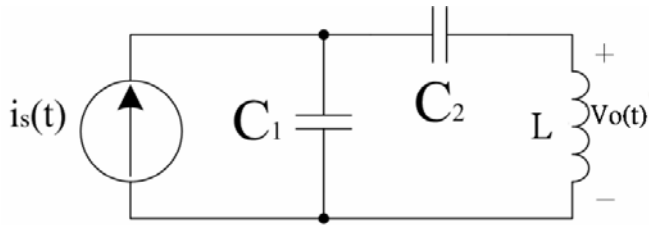


Fig. 7