

國立彰化師範大學 98 學年度碩士班招生考試試題

系所： 電機工程學系

科目： 電子學

☆☆請在答案紙上作答☆☆

第 1 頁，共 4 頁

1. Find the output voltage v_o and the current i_o for the amplifier in Figure 1. Assume the input voltage to be v_I . (10%)

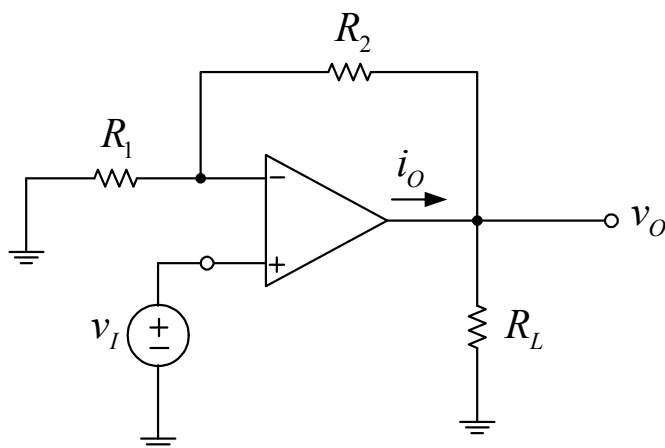


Figure 1

2. Derive an expression in terms of the input voltage V_{IN} for the output voltage V_{OUT} in the circuit of Figure 2. Assume the current of the diode to be $I_D = I_S e^{V_D/nV_T}$. (10%)

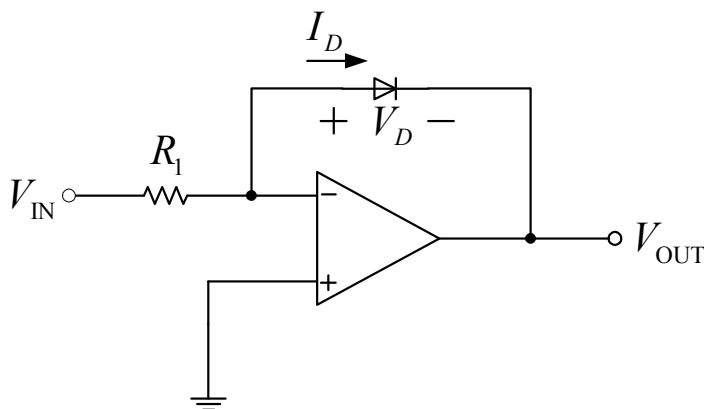


Figure 2

3. In the circuit of Figure 3, the transistor has a β of 100. Find the input resistance R_{in} and the overall voltage gain (v_o/v_{sig}) . (10%)

國立彰化師範大學 98 學年度碩士班招生考試試題

系所： 電機工程學系

科目： 電子學

☆☆請在答案紙上作答☆☆

第 2 頁，共 4 頁

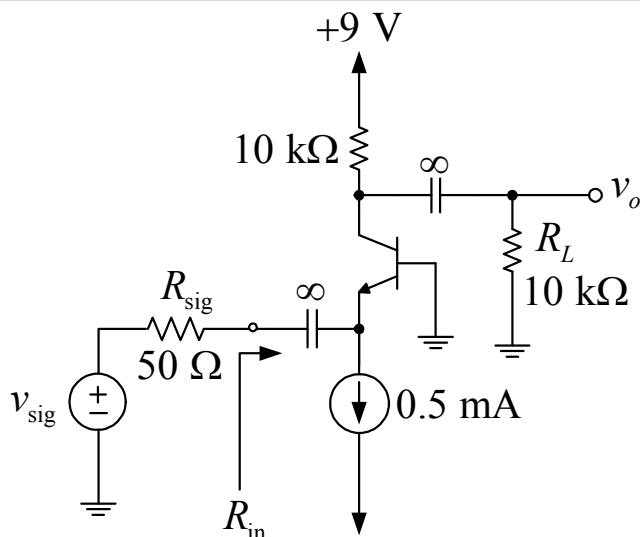


Figure 3

4. Consider the amplifier in Figure 4, and neglect r_o .
- (a) Show that the midband gain is given by $A_M = -g_m R_D / (1 + g_m R_S)$. (10%)
- (b) If the amplifier is biased to operate at $I_D = 1 \text{ mA}$ and $g_m = 1 \text{ mA/V}$, evaluate the midband gain, and the value of C_S that places f_L at 10 Hz. (10%)

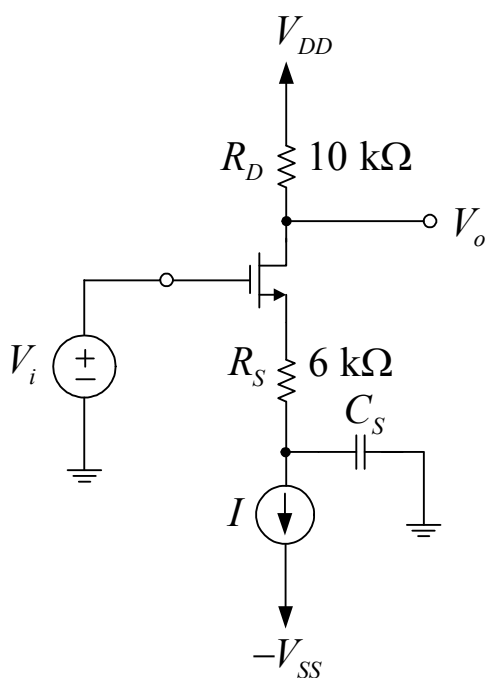


Figure 4

國立彰化師範大學 98 學年度碩士班招生考試試題

系所： 電機工程學系

科目： 電子學

☆☆請在答案紙上作答☆☆

第 3 頁，共 4 頁

5. Consider the differential amplifier in Figure 5. Show that if all transistors have equal transconductances g_m and equal Early voltages $|V_A|$ and are operated at an overdrive voltage V_{OV} , the gain is given by $A_d = 2(V_A/V_{OV})^2$. (10%)

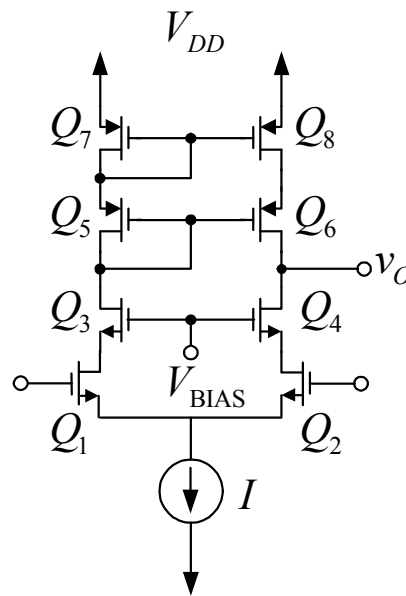


Figure 5

6. The open-loop gain of an amplifier is given by

$$A(f) = \frac{5 \times 10^3}{\left(1 + j \frac{f}{10^4}\right) \left(1 + j \frac{f}{10^5}\right)^2}$$

Assume that the feedback factor β is not a function of frequency.

- (a) Determine the value of β at which the amplifier can break into oscillation. (10%)
- (b) If a phase margin of 45° is required, what should be the value of β ? (10%)
7. It is required to design a class AB output stage in Figure 6 to deliver an average power of 16 W to an 8- Ω load. The peak output voltage is chosen to be no more than 80 percent of V_{CC} . Determine the supply voltage required, the peak current

國立彰化師範大學 98 學年度碩士班招生考試試題

系所： 電機工程學系

科目： 電子學

☆☆請在答案紙上作答☆☆

第 4 頁，共 4 頁

drawn from each supply, the total supply power, and the power-conversion efficiency. (20%)

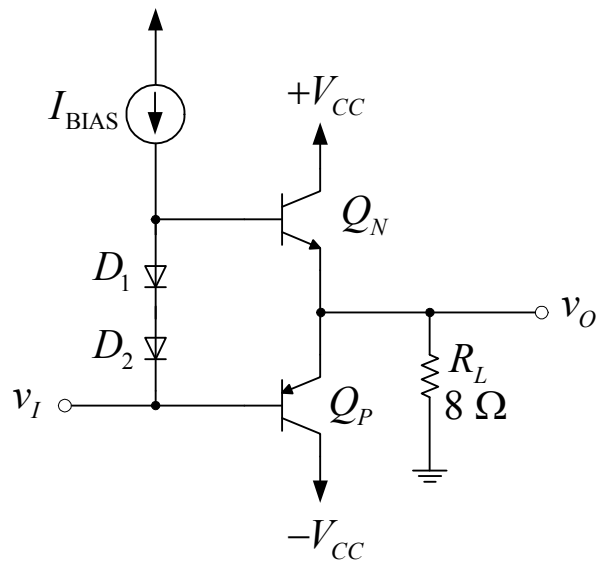


Figure 6