

國立彰化師範大學 96 學年度碩士班招生考試試題

系所：電機工程學系

科目：電子學

☆☆請在答案紙上作答☆☆

共 3 頁，第 1 頁

1. Sketch the voltage transfer characteristics (i.e., v_o vs. v_i) for the circuits in Figure 1. Assume all diodes to be ideal and $V_Z = 5\text{ V}$. (10%)

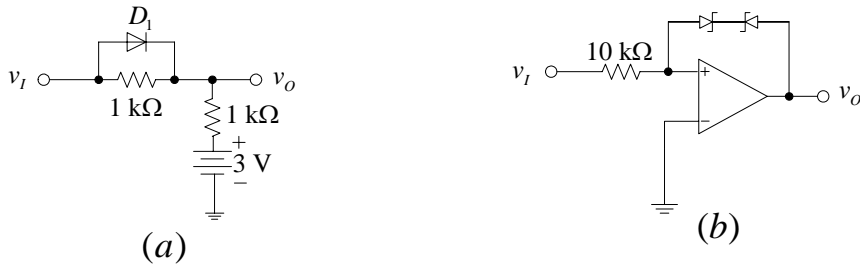


Figure 1

2. Assuming the op amps in Figure 2 (a) and (b) to be ideal, express the output voltage/current (i.e., v_o and i_o) as a function of v_1 and v_2 . (20%)

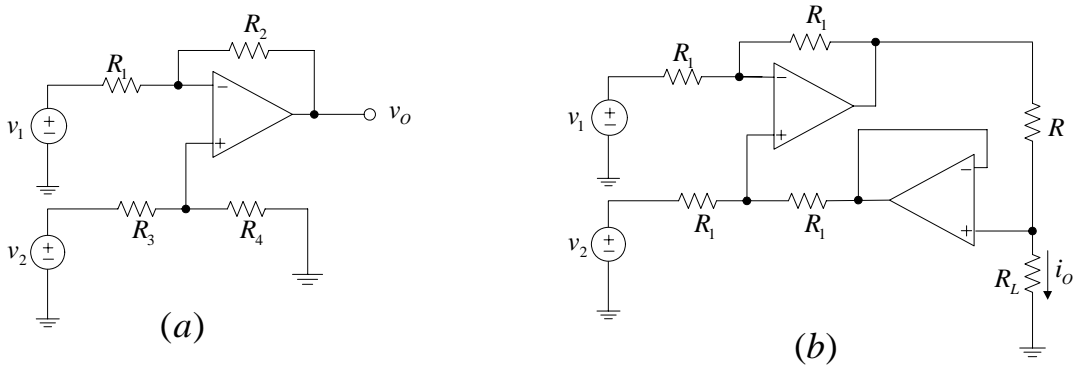


Figure 2

3. (a) Sketch the small-signal equivalent circuit for the CE amplifier in Figure 3. (5%)
 (b) Neglecting the effect of r_o , derive the expressions for the voltage gain v_o/v_s and input resistance R_{in} based on the equivalent circuit in part (a). (10%)

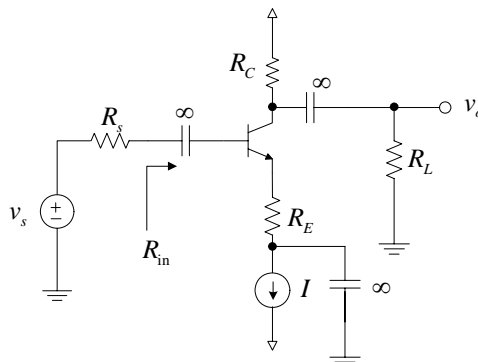


Figure 3

國立彰化師範大學 96 學年度碩士班招生考試試題

系所：電機工程學系

科目：電子學

☆☆請在答案紙上作答☆☆

共 3 頁，第 2 頁

4. The MOSFETs in the circuit of Figure 4 have $V_t = 1\text{ V}$, $\mu_n C_{ox}(W/L) = 1\text{ mA/V}^2$, and $\lambda = 0$. Find:
- The current I , (5%)
 - The range of R such that Q_3 is still in saturation. (5%)

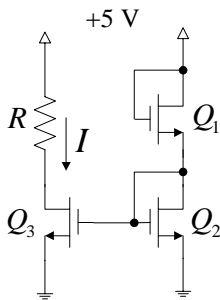


Figure 4

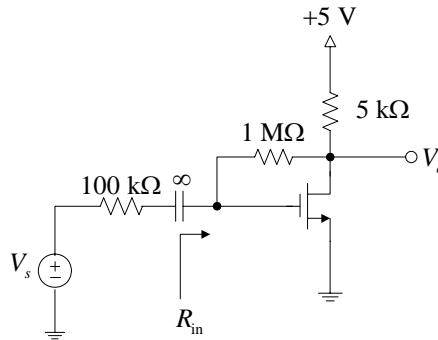


Figure 5

5. The MOS transistor in the feedback network of Figure 5 has $V_t = 1\text{ V}$, $\mu_n C_{ox}(W/L) = 2\text{ mA/V}^2$, $\lambda = 0$. Utilize the feedback analysis method to find:
- The voltage gain V_o/V_s , (10%)
 - The input resistance R_{in} . (5%)
6. The amplifier in Figure 6 has the parameters: $I = 200\ \mu\text{A}$, $V_{OV} = 0.25\text{ V}$, $R_s = 200\text{ k}\Omega$, and $R_D = 50\text{ k}\Omega$. Assuming $\lambda = 0$ for Q_1 and Q_2 , find the low-frequency voltage gain of the amplifier. (10%)

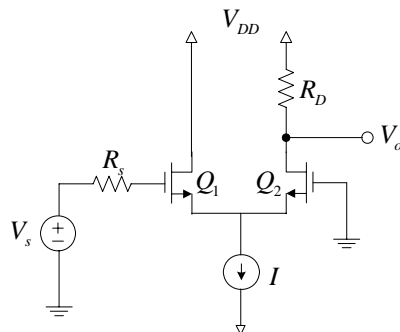


Figure 6

國立彰化師範大學 96 學年度碩士班招生考試試題

系所：電機工程學系

科目：電子學

☆☆請在答案紙上作答☆☆

共 3 頁，第 3 頁

7. Consider the second-order low-pass filter in Figure 7.
- (a) Derive an expression for the filter transfer function. (5%)
 - (b) Find the dc gain. (5%)
 - (c) Find the pole frequency ω_0 . (5%)
 - (d) Find the quality factor Q . (5%)

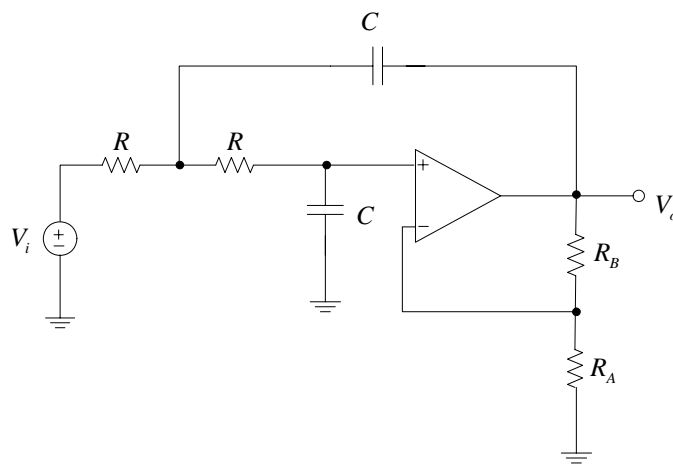


Figure 7