

國立彰化師範大學 98 學年度碩士班招生考試試題





系所：光電科技研究所

科目：乙、電子學

☆☆請在答案紙上作答☆☆

共 2 頁，第 1 頁

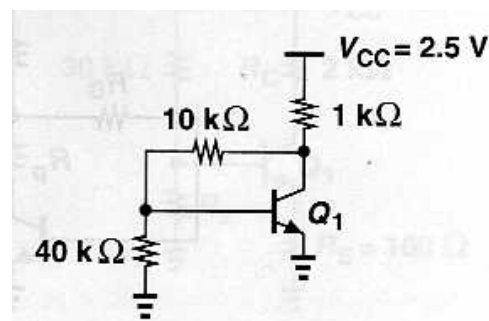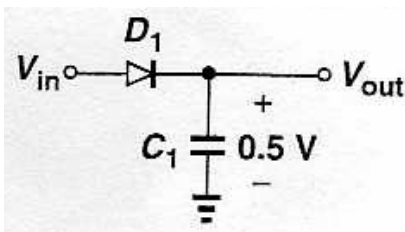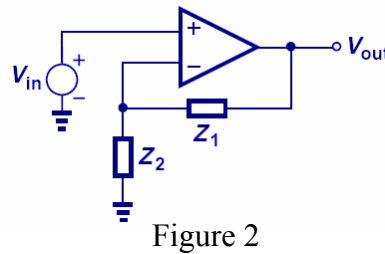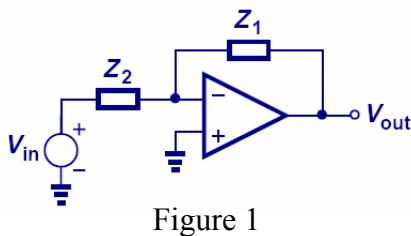- (a) Figure 1 shows the circuit with general impedances around the operational amplifier. $V_{out}/V_{in} = ?$
 (b) Figure 2 shows the circuit with general impedances around the operational amplifier. $V_{out}/V_{in} = ?$ (20%)
- Assuming $V_{in} = V_P \sin \omega t$, plot the output waveform of the circuit depicted in Figure 3 for an initial condition of +0.5 V across C_1 . Assume $V_P = 5$ V. (10%)
- In the circuit of Figure 4, $I_S = 8 \times 10^{-16}$ A, $\beta = 100$, and $V_A = \infty$. (a) Determine the operating point of Q_1 . (b) Draw the small-signal equivalent circuit. (20%)



- Consider an NMOS CG amplifier for which the current-source load is implemented with a PMOS transistor having an output resistance r_o equal to that of the NMOS transistor. Design the circuit to obtain $v_o/v_i = 180$ V/V and $R_{in} = 5$ kΩ. Assume $|V_A| = 20$ V, $\chi = 0.2$, and $k'_n = 120 \mu\text{A}/\text{V}^2$.
 (a) Plot the small signal equivalent circuit (5%).
 (b) Specify I and W/L of the NMOS transistor. (10%).
- For the circuit in Figure 5, let the bias be such that each transistor is operating at 125 μA collector current. Let the BJT have $\beta = 160$, $f_T = 800$ MHz, and $C_{\mu} = 0.2$ pF, and neglect r_o and r_x . Also, $R_{sig} = R_c = 50$ kΩ. (a) Find the low-frequency gain (5%), (b) the high frequency poles (5%), and (c) an estimate of f_H (5%). (d) Finally, Explain the meaning of 3-dB frequency (5%).

國立彰化師範大學 98 學年度碩士班招生考試試題

系所：光電科技研究所

科目：乙、電子學

☆☆請在答案紙上作答☆☆

共 2 頁，第 2 頁

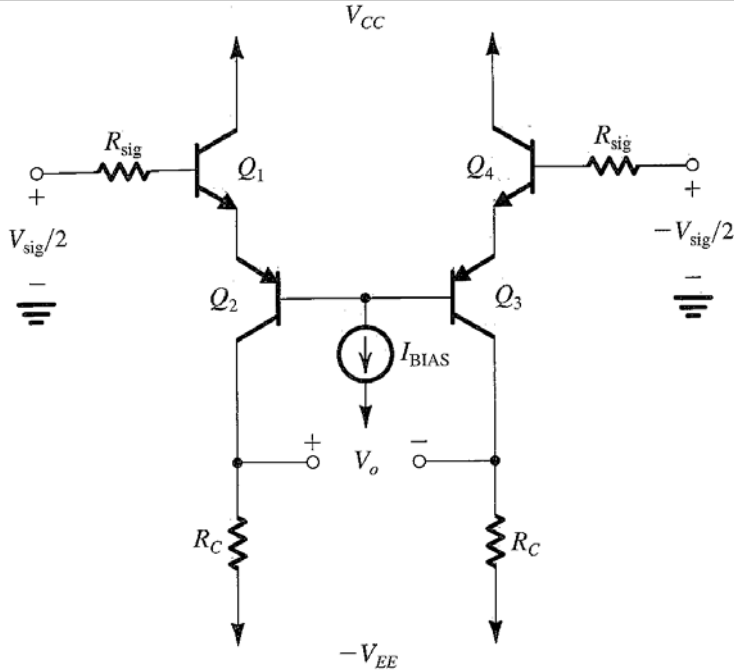


Figure 5

6. In the common gate amplifier circuit of Figure 6, Q_2 and Q_3 are matched, $k'_n (W/L)_n = k'_p (W/L)_p = 5 \text{ mA/V}^2$, and all transistors have $|V_t| = 0.5 \text{ V}$ and $|V_A| = 25 \text{ V}$. Transistor Q_1 has $\chi = 0.2$. The signal v_{sig} is a small sinusoidal signal with no dc component.
- Neglect effect of V_A , find the required value of V_{BIAS} . (5%)
 - Find the values of R_{in} and R_{out} . (5%)
 - Calculate the voltage gain v_o / v_i . (5%).

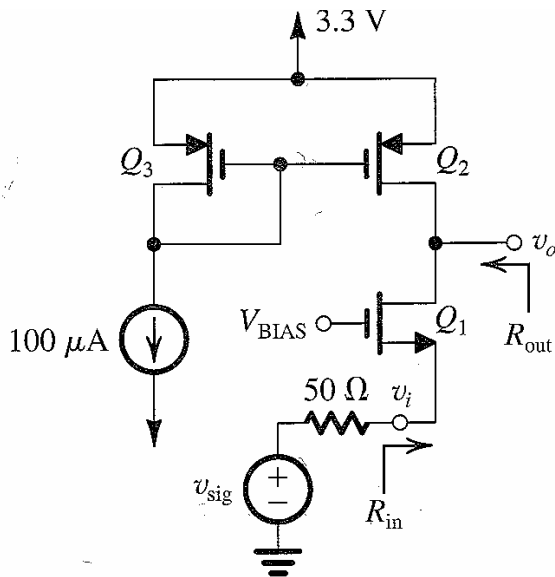


Figure 6