

國立彰化師範大學 95 學年度碩士班招生考試試題

系所： 光電科技研究所

選考： 乙組

科目： 電子學

☆☆請在答案紙上作答☆☆

共 3 頁，第 1 頁

1. Find values for the resistance in the circuit of Fig. 1 with an input resistance of 20 k Ω and a gain of 100. (10%)
2. For the circuit of Fig. 2, use the constant-voltage-drop diode model to find numerical values of the dc component of the output voltage, the peak diode current, and the peak inverse voltage for the case in which v_s is a 12-V (rms) sinusoid, $V_{D0}=0.7$ V, and $R=100\Omega$. [V_{D0} is the intercept on the voltage axis for diodes ($D_1\sim D_4$). D_1 is the same as D_2 , D_3 , or D_4 .] (15%)
3. Please analyze the circuit of Figs. 3, 4, and 5 to determine the voltages at all nodes and the currents through all branches. Which (Figs. 3 or 4) is a bad design? Why? (15%)
4. For the circuit of Fig. 6, let $V_{DD}=V_{SS}=5$ V, $V_{tn}=1$ V, $V_{tp}=-1$ V, all channel lengths = 10 μ m, $k'_n=20\mu$ A/V², $k'_p=8\mu$ A/V², and $\lambda=0$. For $I_{REF}=10\mu$ A, find the widths of all transistors so as to obtain $I_2=50\mu$ A, $I_3=2.5\mu$ A, and $I_5=50\mu$ A. It is further required that the voltage at the drain of Q_2 be allowed to go down to within 0.5V of the negative supply and that the voltage at the drain of Q_5 be allowed to go up to within 0.5V of the positive supply. (15%)
5. For the enhancement-load amplifier. Let $W_1=100\mu$ m, $L_1=6\mu$ m, $W_2=6\mu$ m, $L_2=30\mu$ m. If the body-effect parameter $\chi=0.2$, find the voltage gain without and with the body effect taken into account. Neglect the effect of r_o . (15%)
6. If in the circuit of Fig. 7, A is an ideal voltage amplifier of gain 100 V/V, find A_M , $F_L(s)$, and $F_H(s)$. Also find ω_L , ω_H , and the frequencies at which the gain reduces to unity. [A_M is the magnitude of midband gain in volts per volt. $F_L(s)$ and $F_H(s)$ are functions that account for the dependence of gain on frequency in the low-frequency band and in the high-frequency band, respectively. The extent of the midband is defined by two frequencies ω_L and ω_H .] (15%)
7. Use the feedback method to find the voltage gain V_o/V_s , the input resistance R_{in} , and the output resistance R_{out} of the inverting op-amp configuration of Fig. 8. Let the op amp have open-loop gain $\mu=10^4$ V/V, a differential input resistance $R_{id}=100$ k Ω , and an output resistance $r_o=1$ k Ω . (Hint: The feedback is of shunt-shunt type.) (15%)

題目與圖引用 “Microelectronic Circuits / Sedra and Smith (Oxford 出版)”一書

Fig.1


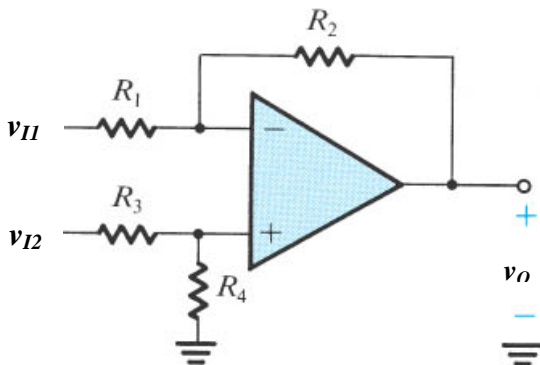


Fig. 2

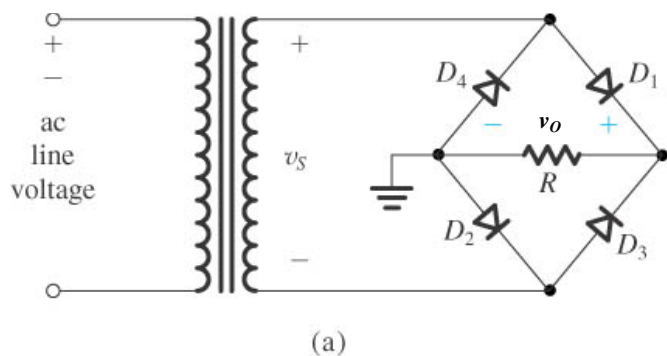

國立彰化師範大學 95 學年度碩士班招生考試試題

系所： 光電科技研究所

選考： 乙組

科目： 電子學

☆☆請在答案紙上作答☆☆

共 3 頁，第 2 頁

Fig.3

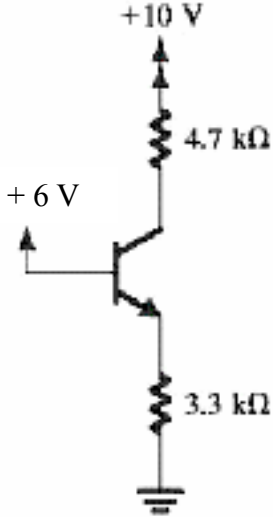


Fig. 4

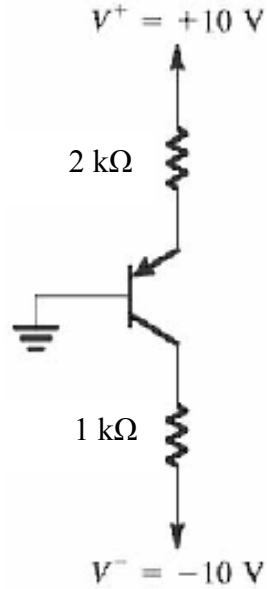


Fig.5


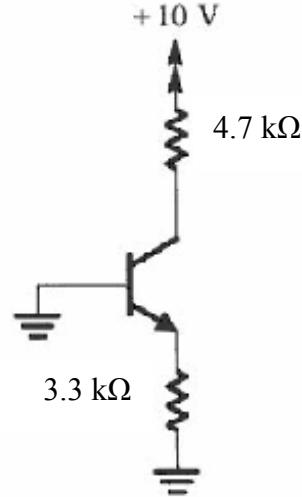


Fig.6

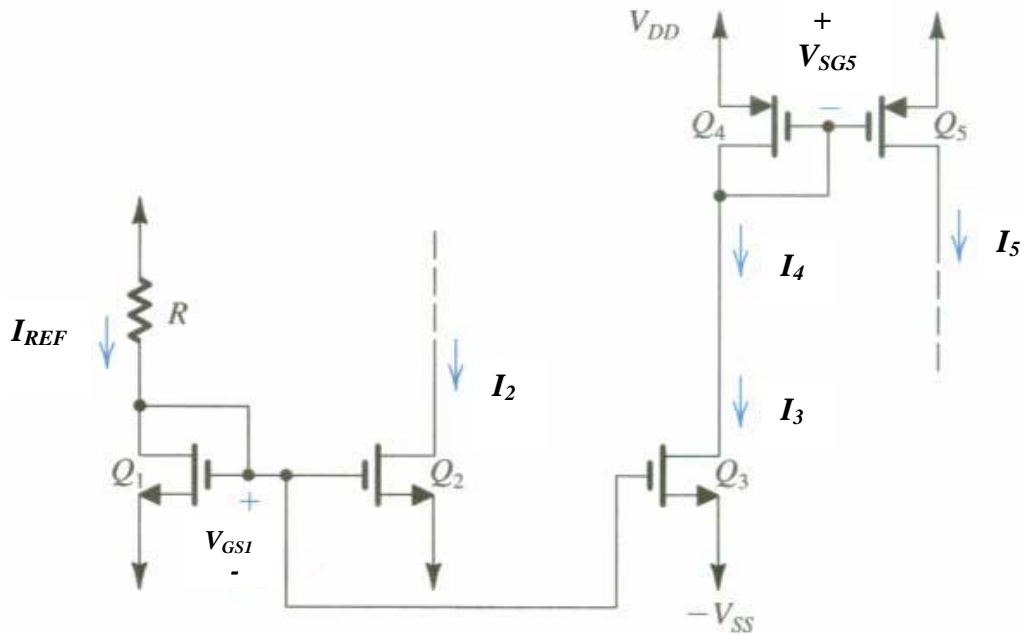

國立彰化師範大學 95 學年度碩士班招生考試試題

系所： 光電科技研究所

選考： 乙組

科目： 電子學

☆☆請在答案紙上作答☆☆

共 3 頁，第 3 頁

Fig.7

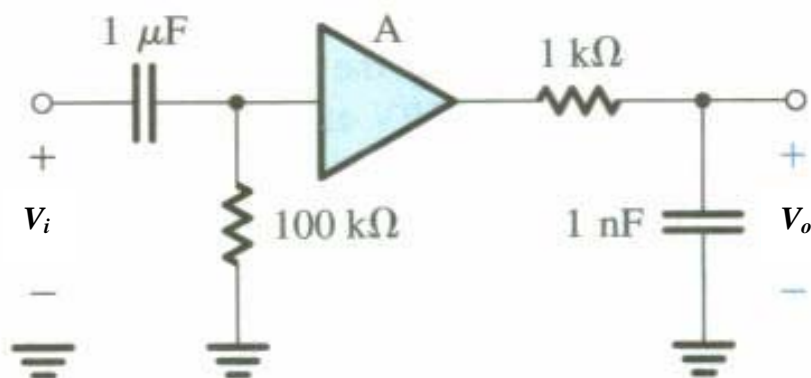


Fig. 8

