

# 國立彰化師範大學 101 學年度碩士班招生考試試題

系所： 車輛科技研究所

科目： 電子學

☆☆請在答案卷上作答☆☆

共 2 頁，第 1 頁

1. Consider a 8-bit digital word  $D=b_7b_6b_5b_4b_3b_2b_1b_0$  used to represent an analog signal  $v_a$  that varies between 0V and +15V. If  $v_a=+5V$ , what do you expect  $D$  to be? What is the resulting error (%) in representation? (20%)

2. For the circuit in Fig. 2 determine the voltage gain  $V_o/V_i$  and current gain  $i_L/i_i$ . (20%)

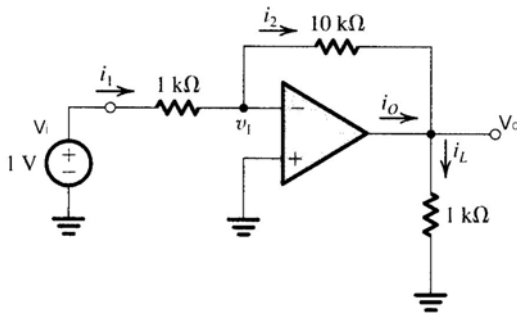


Fig. 2

3. For the wave rectifier circuit in Fig. 3a and 3b, draw the input and output waveform. (10%)

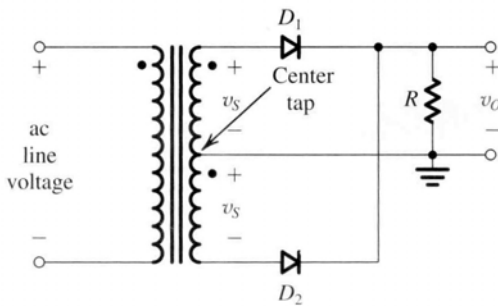


Fig. 3a

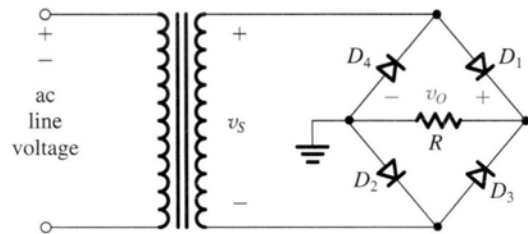


Fig. 3b

4. An enhancement-type NMOS transistor with  $V_t=0.7V$  has its source terminal grounded and a 1.5V dc applied to the gate. In what region does the device operate for (a)  $V_D=+0.5V$ ? (b)  $V_D=+0.9V$ ? (10%)

5. The transistor in Fig. 5 is specified to have  $\beta$  in the range of 50 to 150. Find the value of  $R_B$  that results in saturation with an overdrive factor of at least 20. (20%)

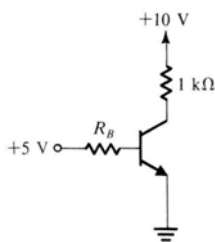


Fig. 5

# 國立彰化師範大學 101 學年度碩士班招生考試試題

系所： 車輛科技研究所

科目： 電子學

☆☆請在答案卷上作答☆☆

共 2 頁，第 2 頁

6. Explain the basic CMOS logic inverter (in Fig. 6a) behaves as an ideal inverter. (5%)  
If the signal source  $v_i$  is shown in Fig. 6b, draw the output waveform of  $v_o$ . (5%)

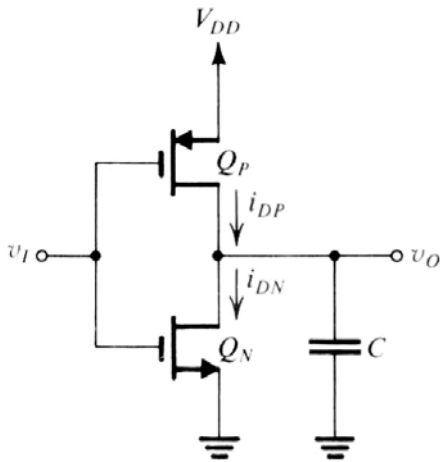


Fig. 6a

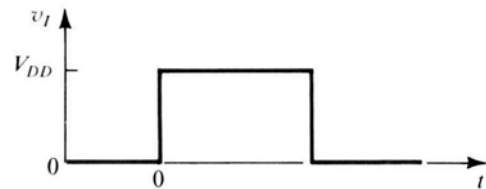


Fig. 6b

7. Explain the following properties of negative feedback: (a) Gain desensitivity (b) bandwidth extension (c) noise reduction (d) reduction in nonlinear distortion. (10%)