

# 國立彰化師範大學103學年度碩士班招生考試試題

系所： 電子工程學系(甲組選考乙、乙組選考丙)、  
資訊工程學系積體電路設計碩士班(選考乙)、  
電信工程學研究所(選考乙)

科目： 電子學


☆☆請在答案紙上作答☆☆

共 2 頁，第 1 頁

1. The shunt regulator circuit uses a Zener diode D which has  $V_z = 7.2\text{ V}$  at  $I_z = 10\text{ mA}$ . The dynamic resistance is  $5\ \Omega$ . The minimum value of  $v_i$  is  $16\text{ V}$ , the maximum value of  $I_L$  is  $25\text{ mA}$ .

(a) If the minimum allowable  $I_z$  is  $5\text{ mA}$ , find the maximum usable value of  $R_s$ . (10%)

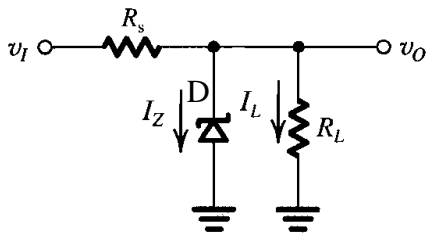(b) Find the line regulation  $\frac{\Delta v_o}{\Delta v_i}$  and the load regulation  $\frac{\Delta v_o}{\Delta I_L}$ . (10%)



2. What is the difference between a p-n diode and a Schottky diode? (10%)

3. Explain the following terminologies.

(a) Channel length modulation. (5%)

(b) Avalanche breakdown. (5%)


4. In the circuit shown below,  $v_{sig}$  is a small sine-wave signal with zero average and  $R_{sig} = 2\text{ k}\Omega$ . The transistor  $\beta$  is 100 and  $V_A = 50\text{ V}$ . ( $V_T = 25\text{ mV}$ )

(a) Find the value of  $R_E$  to establish a dc emitter current of  $1\text{ mA}$ . (5%)

(b) Find the value of  $R_C$  to establish a dc collector voltage of  $-2\text{ V}$ . (5%)

(c) Find  $R_{in}$  and  $R_{out}$ . (10%)

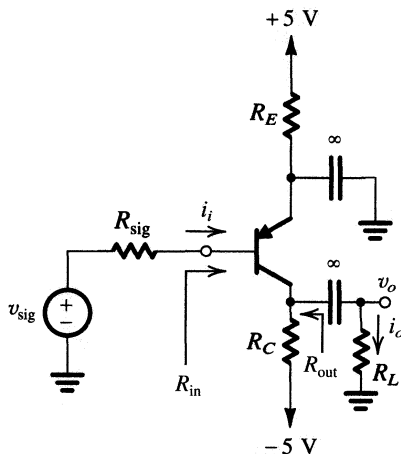(d) For  $R_L = 5\text{ k}\Omega$ , determine the overall voltage gain  $v_o / v_{sig}$ . (10%)



# 國立彰化師範大學103學年度碩士班招生考試試題

系所：電子工程學系(甲組選考乙、乙組選考丙)、  
資訊工程學系積體電路設計碩士班(選考乙)、  
電信工程學研究所(選考乙)

科目：電子學

☆☆請在答案紙上作答☆☆

共 2 頁，第 2 頁

5. The current mirror circuit shown below has  $L_1 = L_2 = 1 \mu\text{m}$ ,  $W_1 = 1 \mu\text{m}$ ,  $V_t = 1 \text{V}$ ,  $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$ ,  $V_A = 20 \text{V}$ ,  $V_{DD} = 5 \text{V}$

- (a) If we want to establish a reference current,  $I_{REF} = 100 \mu\text{A}$ , calculate the value of  $V_{GS}$ , and  $R$ . (10%)
- (b) Find the value of  $W_2$  that will result in  $I_{D2}$  current equal to  $250 \mu\text{A}$  when the drain voltage is equal to the voltage at the gate. (10%)
- (c) If the drain voltage increases by  $5 \text{V}$ , find the resulting value of  $I_{D2}$ . (10%)

