

國立彰化師範大學九十六學年度碩士班招生考試試題

系所：電子工程學系

科目：電子學

請在答案紙上作答

共 1 頁 第 1 頁

- Describe the difference of optical and electric properties between element (Si or Ge) and compound semiconductors (GaAs or GaN). (15%)
- Design a full-wave rectifier for an AC voltage source with  $V_{rms}=110$  V to provide a 15 volt DC voltage. (7%)
  - Design a precision rectifier for instrumentation applications to rectify a signal with small amplitude of 0.1 V. (8%)
- For an enhancement-type n-channel MOSFET,
  - derivate its  $i_D$ - $V_{DS}$  relationship in the triode region, (10%)
  - sketch its characteristic curves and define the three distinct regions of operation. (10%)
- In Fig. 1 transistor  $Q_1$ , biasing arrangement is not shown, is operating as a CE amplifier with an active load provided by  $Q_2$ . Transistors  $Q_2$  and  $Q_3$  form a current mirror. Neglecting the base currents of  $Q_2$  and  $Q_3$  and assuming their  $V_{BE}=0.7$  V and that  $Q_2$  has five times the area of  $Q_3$ ,
  - find the value of  $I$ , (10%)
  - find  $R_{in}$  from  $V_i$  and  $A_v = \frac{V_o}{V_i}$ . (10%)
- Starting from first principles and assuming ideal op amps, derive the transfer function ( $V_o/V_i$ ) of the circuit in Fig. 2. (15%)
- Realize a two-to-one multiplexer using pass-transistor logic. (15%)

Fig. 1

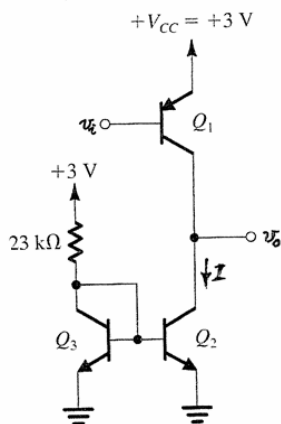


Fig. 2

