

國立彰化師範大學 100 學年度碩士班招生考試試題


系所：資訊工程學系積體電路設計碩士班

科目：電子學


☆☆請在答案紙上作答☆☆

共 2 頁，第 1 頁

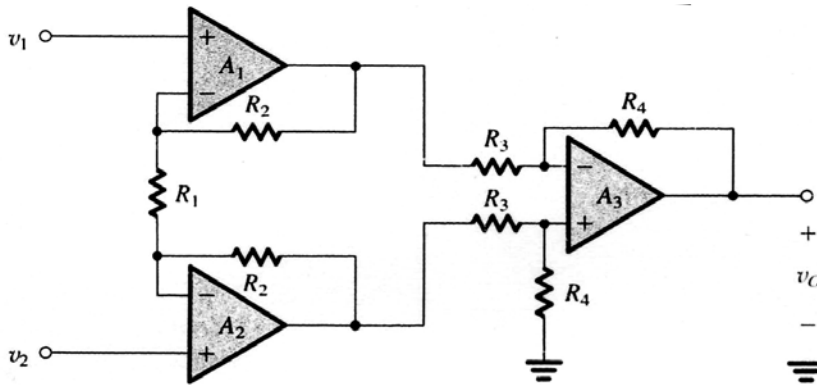1. (15%) For the circuit shown in the following figure, express v_o as a function of v_1 and v_2 . Assume all op amps are ideal operational amplifiers.



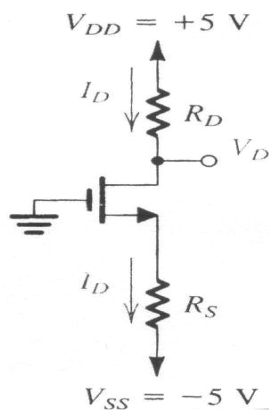2. (15%) For a pn junction with $N_A = 10^{17}/\text{cm}^3$ and $N_D = 10^{16}/\text{cm}^3$, find, at $T = 300$ K, the built-in voltage, the width of the depletion region, and the distance it extends in the p side and the n side of the junction. Use $n_i = 1.5 \times 10^{10}/\text{cm}^3$, $\epsilon_s = 1.04 \times 10^{-12}$ F/cm, $V_T = 25$ mV.
3. (20%) Design the values of R_D and R_S for the following circuit so that the transistor operates at $I_D = 0.4$ mA and $V_D = +1$ V. The NMOS transistor has $V_t = 2$ V, $\mu_n C_{ox} = 20 \mu\text{A}/\text{V}^2$, $L = 10 \mu\text{m}$, and $W = 400 \mu\text{m}$. Neglect the channel-length modulation effect.



國立彰化師範大學 100 學年度碩士班招生考試試題


系所：資訊工程學系積體電路設計碩士班

科目：電子學


☆☆請在答案紙上作答☆☆

共 2 頁，第 2 頁

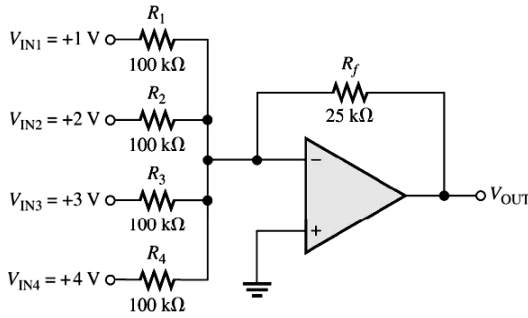4. (15%) What is the output voltage for the averaging amplifier in the following figure.



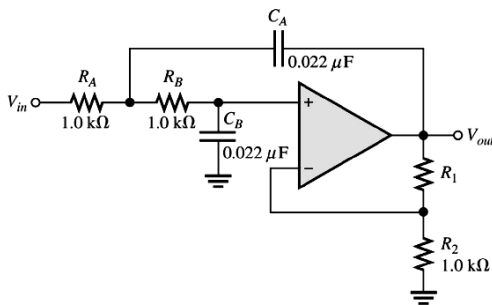5. (15%) Determine the critical frequency of the Sallen-Key low-pass filter in the following figure and set the value of R1 for an approximate Butterworth response.



6. For the amplifier in the following figure. ($V_{in} = 10 \text{ mV}$)

甲、Determine the dc collector voltage. (10%)

乙、Determine the ac collector voltage. (10%)

