

國立彰化師範大學 98 學年度碩士班招生考試試題

系所： 積體電路設計研究所

科目： 電子學

☆☆請在答案紙上作答☆☆

共 2 頁，第 1 頁

1. Design a Widlar current source of Fig.1 to generate a current $I_{C1}=10\mu\text{A}$ given that $I_{REF}=0.2\text{ mA}$. If for the transistors, $I_S=2\times 10^{-14}\text{ A}$, find V_{BE2} and V_{BE1} . Assume β to be high. (15%)


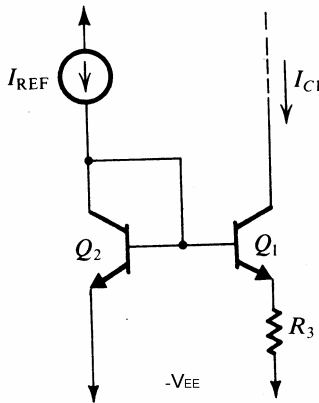


Fig. 1

2. An amplifier has a dc gain of 10^4 V/V and poles at 10^4 Hz , $2\times 10^4\text{ Hz}$, and 10^5 Hz . Find the value of feedback factor (β), and the corresponding closed-loop gain, for which a phase margin of 50° is obtained. (15%)
3. Design a pseudo-NMOS inverter that has $V_{OL}=0.15\text{V}$. Let $V_{DD}=3.3\text{V}$, $|V_t|=0.5\text{V}$, $k'_n=2k'_p=100\mu\text{A/V}^2$, and $(W/L)_n=0.7\mu\text{m}/0.35\mu\text{m}$. What is the value of $(W/L)_p$? Calculate the value of NM_L and the static power dissipation. (20%)
4. Assume the diode is ideal. Sketch the output v_o for the input shown below. Label the most positive and most negative output levels. (14%)

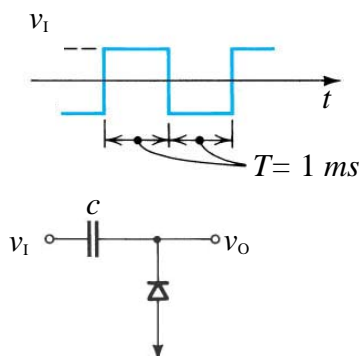

國立彰化師範大學 98 學年度碩士班招生考試試題


系所：積體電路設計研究所

科目：電子學


☆☆請在答案紙上作答☆☆

共 2 頁，第 2 頁

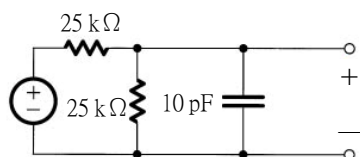5. Find the dc transmission, the corner frequency f_0 , and the transmission at $f = 8 \text{ MHz}$ for the circuit. (24 %)



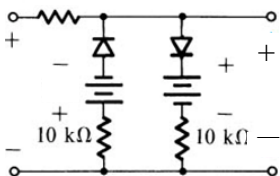6. Assuming the diodes to be ideal, find the transfer characteristic of the circuit. (12 %)



V_i

V_o

$5 \text{ k}\Omega$

$V_i \quad 3 \text{ V}$

$3 \text{ V} \quad V_o$