

國立彰化師範大學 102 學年度碩士班招生考試試題

系所：電信工程學研究所

選考甲

科目：電子學

☆☆請在答案紙上作答☆☆

共 1 頁，第 1 頁

1. From Fig. 1 find v_x/v_i and v_o/v_i . (20%)

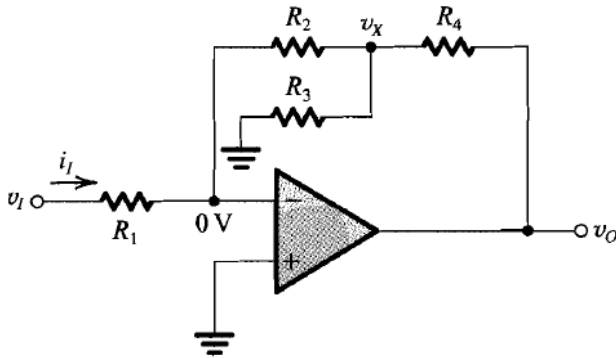


Fig. 1.

2. A diode has a 0.7-V drop at a current of 2 mA and $n = 2$. What is the diode conducting current at $V_D = 0.8$ V, and what is the diode voltage drop at $I_D = 10$ mA? (20%)
3. A CE amplifier utilizes a BJT with $\beta = 100$ and $V_A = 50$ V, biased at $I_C = 0.5$ mA; it has a collector resistance $R_C = 10$ k Ω , a resistance $R_E = 100$ Ω is connected in the emitter. Find R_{in} , A_{vo} and R_o . (20%)
4. An NMOS differential pair is biased by a current source $I = 0.2$ mA having an output resistance $R_{CS} = 200$ k Ω . The amplifier has drain resistances $R_D = 20$ k Ω , using transistors with $k'_n = 200$ $\mu\text{A/V}$, $W/L = 10$, and neglecting r_o . If the output is taken differentially and there is a 2% mismatch between the drain resistances, find $|A_d|$, $|A_{cm}|$, and CMRR. (20%)
5. A common-source amplifier has $R_{in} = 200$ k Ω , $R_D = 10$ k Ω . The transistor has $g_m = 2$ mA/V, $r_o = 100$ k Ω , $C_{gs} = 1.5$ pF, and $C_{gd} = 0.5$ pF. The amplifier is fed from a voltage source v_s with an internal resistance of 200 k Ω and is connected to a 10 k Ω load.
Find: (a) the overall midband voltage gain $A_M = v_o/v_s$. (b) the upper 3-dB frequency f_H . (20%)