

# 國立彰化師範大學 98 學年度碩士班招生考試試題

系所：顯示技術研究所

科目：甲、電子學

☆☆請在答案紙上作答☆☆

共 1 頁，第 1 頁

1. At room temperature, a diode for which  $n=1$  operates in a circuit for which the current is essentially a constant value of 1 mA. Find the corresponding diode incremental resistance. (10%)

2. For the circuit as shown in Figure 1, find the labeled node voltages.  $\beta=100$ . (20%)

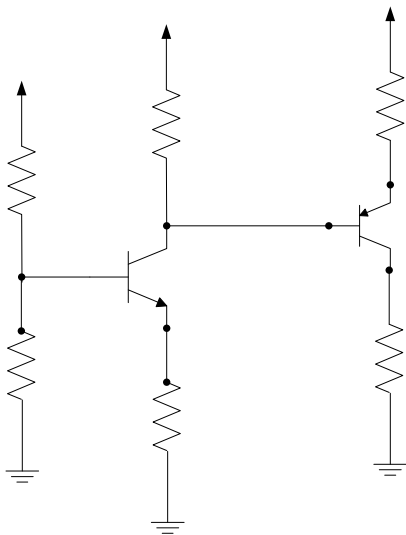


Figure 1

3. An amplifier has the voltage transfer function

$$T(s) = \frac{10s}{(1 + s/100)(1 + s/10000)}$$

+15 V

- (a) Find the poles and zeros. (5%)

- (b) Sketch the magnitude of the gain versus frequency. (10%)

- (c) Find approximate values for the gain at  $\omega = 10, 10^2, \text{ and } 10^6 \text{ rad/s}$ . (15%)

4. Design a NAND logic gate using BJTs. (15%)

10 k $\Omega$

5. Explain the Wilson current mirror. (10%)

200 k $\Omega$

V<sub>3</sub>

6. Draw and explain the transfer characteristics of a CMOS inverter. (15%)

1 k $\Omega$

V<sub>4</sub>

V<sub>1</sub>

V<sub>5</sub>