請在答案紙上作答

共<u>1</u>頁 第<u>1</u>頁

每題十分。總分一佰分。

9.

1. Find the transfer function relating the capacitor voltage, $V_{C(s)}$, to the input voltage, V(s), in the figure.



Compute both the Fourier sine and cosine integrals of $f(x) =$	$\int 2x + 1$,	$0 \le x \le \pi$
	2,	$\pi \le x \le 3\pi$
] 1,	$3\pi \le x \le 10\pi$
	0.	$x > 10\pi$

10. Let *A* and *B* be symmetric, $n \times n$ matrices. Prove that, in general, *AB* is symmetric if and only if AB = BA.